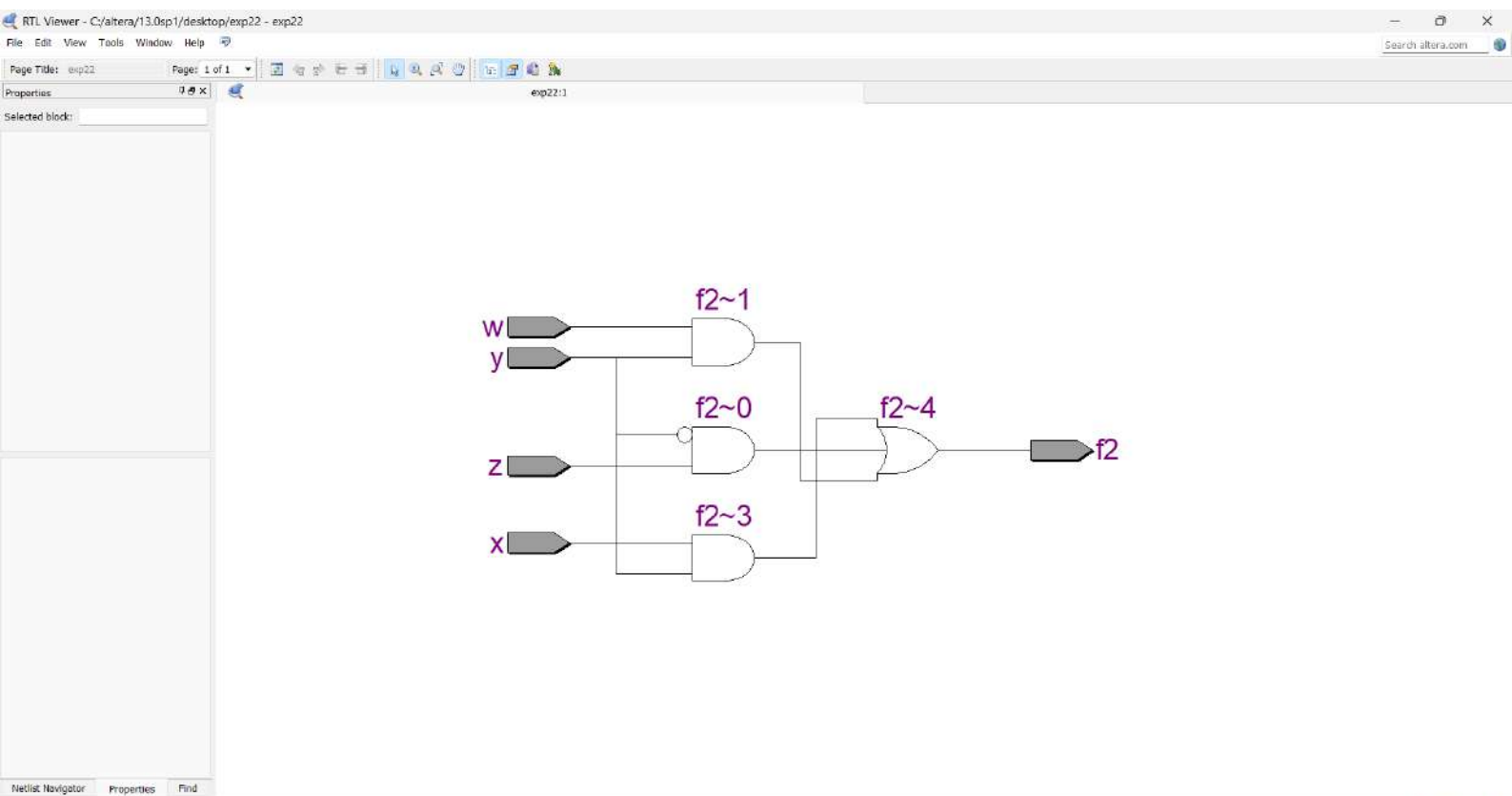
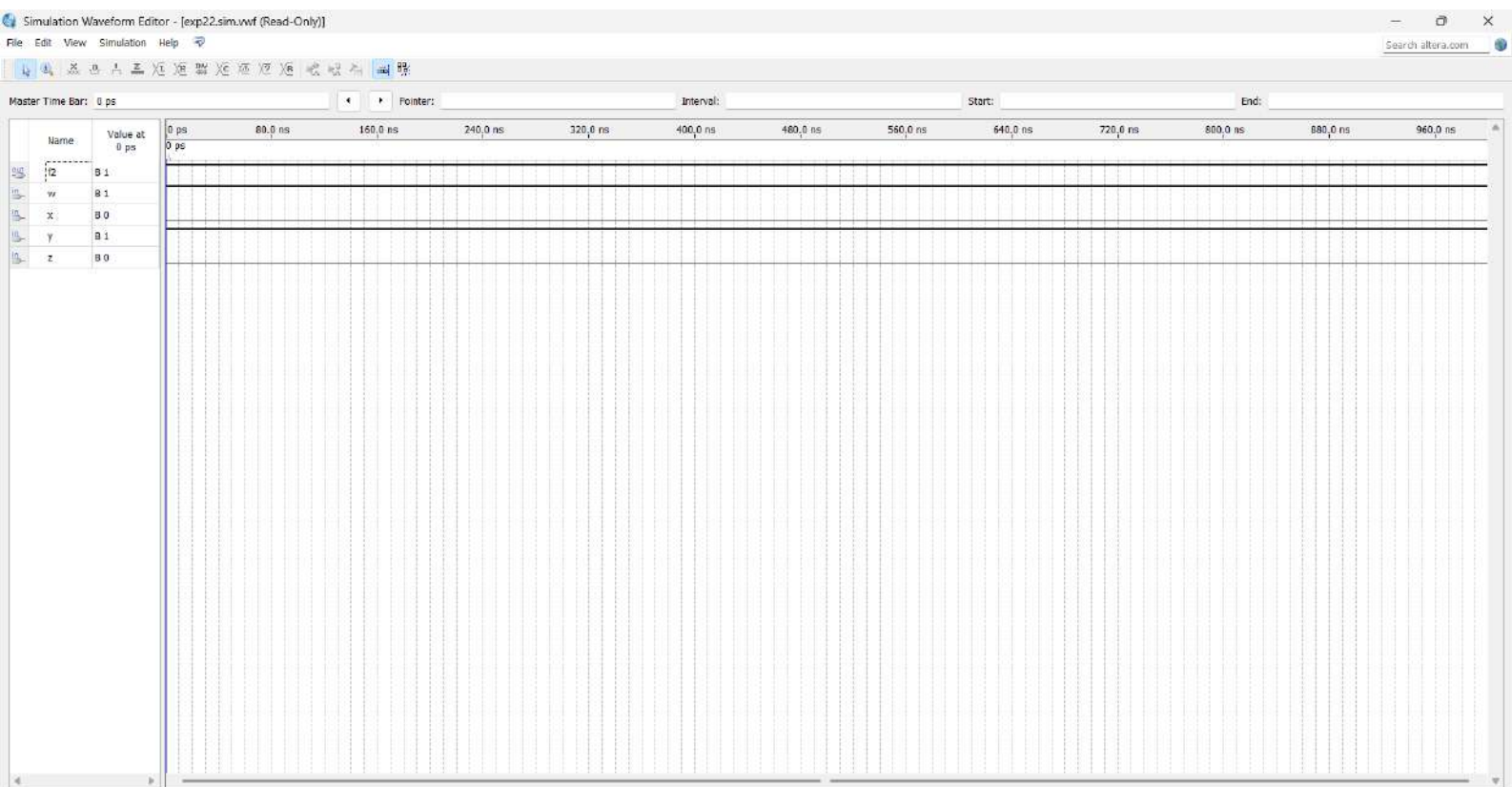






RTL Viewer - C:/altera/13.0sp1/desktop/exp2 folder/exp2 - exp2

File Edit View Tools Window Help

Page Title: exp2 Page: 1 of 1

Properties exp2:1

Selected block:

The diagram illustrates a logic circuit with four inputs: **a**, **b**, **c**, and **d**. The circuit consists of three 2-input AND gates and one 3-input OR gate. The first AND gate, labeled **f1~0**, takes inputs **b** and **d**. The second AND gate, labeled **f1~2**, takes inputs **a** and **d**. The third AND gate, labeled **f1~5**, takes inputs **a** and **c**. The outputs of these three AND gates are connected to a 3-input OR gate, labeled **f1~6**. The final output of the OR gate is **f1**.

Netlist Navigator Properties Find

CAD/INR +0.83%

Search

100% 00:00:01

ENG IN 22:00 21-11-2025

